

VLSI System Design

ELE301P

LAB - 5 - Report

Praveen B R

COE19B007

Submission Date: 12/10/2021

# INDEX

- ❖ Q1) Flip-Flops
  - SR Flip-flop
    - Code
    - Output/Waveform
  - JK Flip-flop
    - Code
    - Output/Waveform
  - D Flip-flop
    - Code
    - Output/Waveform
  - T Flip-flop
    - Code
    - Output/Waveform
- ❖ Q2) Mod 9 Counter
  - Theory
  - Code
  - Output/Waveform
- ❖ Other Questions
  - Question 1
  - Question 2
  - Question 3

## Q1) Flip-Flops

### **Objective:**


To implement a SR, JK, D, T Flip-flops in Verilog using Behavioural Modelling

**Theory:**

Flip-flop is a circuit that maintains a state until directed by input to change the state. A basic flip-flop can be constructed using four-NAND or four-NOR gates.

Types of flip-flops:

- SR Flip Flop
- JK Flip Flop
- D Flip Flop
- T Flip Flop

 **SR Flip-flop:****TRUTH TABLE**

S	R	$Q_N$	$Q_{N+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

**Code**

```
module sr_flipflop(S,R,clock,reset,Q);
    input wire S,R,clock,reset;
    output reg Q;

    always @(posedge clock) begin
        if(reset) begin
            Q<= 1'b0;
        end
        else begin
```

```

        case({S,R})
            2'b00: begin
                Q<=Q;
            end
            2'b01: begin
                Q<=1'b0;
            end
            2'b10: begin
                Q<=1'b1;
            end
            default: begin
                Q<=1'bx;
            end
        endcase
    end
end
endmodule

module SR_ff_tb();

    reg S,R,clock,reset;
    wire Q;

    always begin
        #10 clock=~clock;
    end

    initial begin
        S=0;R=0;reset=1; clock=1;
        #20 S=0;R=0;reset=0;
        #20 S=0;R=1;reset=0;
        #20 S=1;R=0;reset=0;
        #20 S=1;R=1;reset=0;
        #20
        $finish;
    end

    initial begin
        $monitor("S =%b R = %b Clock = %b reset = %b Q =
%b",S,R,clock,reset,Q);
    end

```

```

end

sr_flipflop SRFF1 (S,R,clock,reset,Q);

initial begin
    $dumpfile("SRFF1.vcd");
    $dumpvars(0,SRFF1);
end
endmodule;


```


### Output/Waveform

```

PS E:\Sem 5\VLSI\Lab\lab5> iverilog q1SR.v
PS E:\Sem 5\VLSI\Lab\lab5> vvp a.out
VCD info: dumpfile SR.vcd opened for output.
S =0    R = 0    Clock = 1    reset = 1    Q = 0
S =0    R = 0    Clock = 1    reset = 0    Q = 0
S =0    R = 1    Clock = 0    reset = 0    Q = 0
S =1    R = 0    Clock = 0    reset = 0    Q = 0
S =1    R = 1    Clock = 1    reset = 0    Q = x
q1SR.v:44: $finish called at 25 (1s)
PS E:\Sem 5\VLSI\Lab\lab5> 

```

 

 **JK Flip-flop:****TRUTH TABLE**

J	K	$Q_N$	$Q_{N+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

**Code**

```

module jk_flipflop(J,K,clock,reset,Q);
    input wire J,K,clock,reset;
    output reg Q;

    always @(posedge clock) begin
        if(reset) begin
            Q<= 1'b0;
        end
        else begin
            case({J,K})
                2'b00: begin
                    Q<=Q;
                end
                2'b01: begin
                    Q<=1'b0;
                end
                2'b10: begin
                    Q<=1'b1;
                end
            endcase
        end
    end

```

```

        end
        2'b11: begin
            Q<=~Q;
        end
    endcase
end
end
endmodule

module JK_ff_tb();

    reg J,K,clock,reset;
    wire Q;

    always begin
        #10 clock=~clock;
    end

    initial begin
        J=0;K=0;reset=1; clock=1;
        #5 J=0;K=0;reset=0;
        #5 J=0;K=1;reset=0;
        #5 J=1;K=0;reset=0;
        #5 J=1;K=1;reset=0;
        #5
        $finish;
    end

    initial begin
        $monitor("J =%b \tK = %b \tClock = %b \treset = %b \tQ =
%b",J,K,clock,reset,Q);
    end


    jk_flipflop JKFF (J,K,clock,reset,Q);

    initial begin
        $dumpfile("JK.vcd");
        $dumpvars(0,JKFF);
    end
endmodule;


```
 
## Output/Waveform

```
PS E:\Sem 5\VLSI\Lab\lab5> iverilog q1JK.v
PS E:\Sem 5\VLSI\Lab\lab5> vvp a.out
VCD info: dumpfile JK.vcd opened for output.
J =0    K = 0    Clock = 1    reset = 1    Q = 0
J =0    K = 0    Clock = 1    reset = 0    Q = 0
J =0    K = 1    Clock = 0    reset = 0    Q = 0
J =1    K = 0    Clock = 0    reset = 0    Q = 0
J =1    K = 1    Clock = 1    reset = 0    Q = 1
q1JK.v:44: $finish called at 25 (1s)
```



## D Flip-flop:

 

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

## Code

```
module d_flipflop(D,clock,reset,Q) ;
    input wire D,clock,reset;
    output reg Q;

    always @(posedge clock) begin
```



```

        if(reset) begin
            Q<=1'b0;
        end
        else begin
            Q<=D;
        end
    end
end
endmodule

module D_ff_tb();

    reg D,clock,reset;
    wire Q;

    always begin
        #10 clock=~clock;
    end

    initial begin
        D=0;reset=1; clock=1;
        #20 D=0;reset=0;
        #20 D=1;reset=0;
        #20
        $finish;
    end

    initial begin
        $monitor("D = %b Clock = %b reset = %b Q = %b",D,clock,reset,Q);
    end


    d_flipflop DFF1 (D,clock,reset,Q);

    initial begin
        $dumpfile("DFF1.vcd");
        $dumpvars(0,DFF1);
    end
endmodule;


```
 
## Output/Waveform

```
PS E:\Sem 5\VLSI\Lab\lab5> iverilog q1D.v
PS E:\Sem 5\VLSI\Lab\lab5> vvp a.out
VCD info: dumpfile D.vcd opened for output.
D = 0 Clock = 1 reset = 1 Q = 0
D = 0 Clock = 0 reset = 1 Q = 0
D = 0 Clock = 1 reset = 0 Q = 0
D = 0 Clock = 0 reset = 0 Q = 0
D = 1 Clock = 1 reset = 0 Q = 1
D = 1 Clock = 0 reset = 0 Q = 1
q1D.v:29: $finish called at 60 (1s)
```



## T Flip-flop:

 

$T$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

## Code

```
module t_flipflop(T, clock, reset, Q);
    input wire T, clock, reset;
    output reg Q;
    always @(posedge clock) ebegin
        if(rst) begin
            Q<=1'b0;
        end
    end
```

```

        else begin
            case(T)
                1'b0: begin
                    Q<=Q;
                end
                1'b1: begin
                    Q<=~Q;
                end
            endcase
        end
    end
end
endmodule

module T_ff_tb();

    reg T,clock,reset;
    wire Q;

    always begin
        #10 clock=~clock;
    end

    initial begin
        T=0;rst=1; clock=1;e
        #20 T=0;rst=0;
        #20 T=1;rst=0;
        #20
        $finish;
    end

    initial begin
        $monitor("T = %b Clock = %b rst = %b Q = %b",T,clock,reset,Q);
    end


    t_flipflop TFF (T,clock,reset,Q);

    initial begin
        $dumpfile("T.vcd");
        $dumpvars(0,TFF);
    end
endmodule;

```
 
### Output/Waveform

```
PS E:\Sem 5\VLSI\Lab\lab5> iverilog q1T.v
PS E:\Sem 5\VLSI\Lab\lab5> vvp a.out
VCD info: dumpfile T.vcd opened for output.
T = 0 Clock = 1 reset = 1 Q = 0
T = 0 Clock = 0 reset = 1 Q = 0
T = 0 Clock = 1 reset = 0 Q = 0
T = 0 Clock = 0 reset = 0 Q = 0
T = 1 Clock = 1 reset = 0 Q = 1
T = 1 Clock = 0 reset = 0 Q = 1
q1T.v:36: $finish called at 60 (1s)
```



### Conclusion:

Thus, flip-flops have been implemented successfully in verilog

### Application:

These are the various types of flip-flops being used in digital electronic circuits and the applications of Flip-flops are as specified below.

#### Counters

- Frequency Dividers
- Shift Registers
- Storage Registers
- Bounce elimination switch
- Data storage
- Data transfer
- Latch
- Registers
- Memory

## Q2) Mod 9 Counter

### Objective:

To implement a Mod 9 counter in verilog using Structural Modelling

### Theory:

Counter is a sequential circuit. A digital circuit which is used for a counting pulses is known counter. Counter is the widest application of flip-flops. It is a group of flip-flops with a clock signal applied. Counters are of two types.

- Asynchronous or ripple counters.
- Synchronous counters.

For designing Mod 9 Counter I chose to use T Flip Flop.

Excitation Table of T Flip Flop

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

State Input Table for mod 9 counter

Present State				Next State				Input			
$P_4$	$P_3$	$P_2$	$P_1$	$N_4$	$N_3$	$N_2$	$N_1$	$T_4$	$T_3$	$T_2$	$T_1$
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	1	0	0	0

Now using the input values and draw k-maps,

	00	10	11	10
00				
10			1	
11	x	x	x	x
10	1	x	x	x

$$T_4 = Q_4 + Q_3 \cdot Q_2 \cdot Q_1$$

	00	10	11	10
00			1	
10			1	
11	x	x	x	x
10		x	x	x

$$T_3 = Q_2 \cdot Q_1$$

	00	10	11	10
00		1	1	
10		1	1	
11	x	x	x	x
10		x	x	x

$$T_2 = Q_1$$

	00	10	11	10
00	1	1	1	1
10	1	1	1	1
11	x	x	x	x
10		x	x	x

$$T_1 = Q_4'$$

Then implement the obtained equations in verilog structural style

**Code:**

```
module t_flipflop(T, clock, reset, Q);
input wire T, clock, reset;
output reg Q;

always @(posedge clock) begin
    if(reset) begin
        Q<=1'b0;
    end
    else begin
        case(T)
            1'b0: begin
                Q<=Q;
            end
            1'b1: begin
                Q<=~Q;
            end
        endcase
    end
end
endmodule
```

```

module mod9_Counter(reset,Q,clock);
input clock,reset;
output [3:0] Q;
wire t1,t2,t3;
and(t1,Q[0],Q[1]);
and(t2,t1,Q[2]);
or(t3,t2,Q[3]);

t_flipflop T_1(~Q[3],clock,reset,Q[0]);
t_flipflop T_2(Q[0],clock,reset,Q[1]);
t_flipflop T_3(t1,clock,reset,Q[2]);
t_flipflop T_4(t3,clock,reset,Q[3]);
endmodule

module mod9_tb;
reg clock,reset;
wire [3:0] Q;
mod9_Counter M1(reset,Q,clock);
initial
begin
    #0 clock = 1;reset = 1;
    #1 reset = 0;
    #50 $finish;
end
always
begin
    #2 clock = ~clock;
end
initial
begin
    $monitor($time," \tQ = %d \tclock = %b",Q,clock);
end
initial
begin
    $dumpfile("mod_9.vcd");
    $dumpvars(0,mod9_tb);
end
endmodule


```

**Output/Waveform:**

```

q2mod9.v:49: error: malformed statement
PS E:\Sem 5\VLSI\Lab\lab5> iverilog q2mod9.v
PS E:\Sem 5\VLSI\Lab\lab5> vvp a.out
VCD info: dumpfile mod_9.vcd opened for output.
      0 Q = 0 clock = 1
      2 Q = 0 clock = 0
      4 Q = 1 clock = 1
      6 Q = 1 clock = 0
      8 Q = 2 clock = 1
     10 Q = 2 clock = 0
     12 Q = 3 clock = 1
     14 Q = 3 clock = 0
     16 Q = 4 clock = 1
     18 Q = 4 clock = 0
     20 Q = 5 clock = 1
     22 Q = 5 clock = 0
     24 Q = 6 clock = 1
     26 Q = 6 clock = 0
     28 Q = 7 clock = 1
     30 Q = 7 clock = 0
     32 Q = 8 clock = 1
     34 Q = 8 clock = 0
     36 Q = 0 clock = 1
     38 Q = 0 clock = 0
     40 Q = 1 clock = 1
     42 Q = 1 clock = 0
     44 Q = 2 clock = 1
     46 Q = 2 clock = 0
     48 Q = 3 clock = 1
     50 Q = 3 clock = 0
q2mod9.v:45: $finish called at 51 (1s)

```

 **Conclusion:**

Thus a mod 9 counter has been implemented successfully

**Applications:**

- Alarm Clock
- Set AC Timer
- Set time in camera to take the picture
- Flashing light indicator in automobiles
- Car parking control



## Other Questions

### Question 1

$J = Q_n'$  and  $K=1$

Output table will be and characteristic table of JK flip flop will be:

CLK	$J = \bar{Q}$	$K=1$	$Q_{n+1}$
0	-	-	0
1	1	1	1
2	1	1	1
3	1	1	1

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

With this, we can say that the sequence will be..

1st  $J = 1$ ,  $K = 1 \rightarrow Q = 1, Q' = 0$

2nd  $J = 0$ ,  $K = 1 \rightarrow Q = 0, Q' = 1$

3rd  $J = 1$ ,  $K = 1 \rightarrow Q = 1, Q' = 0$

4th  $J = 0$ ,  $K = 1 \rightarrow Q = 0, Q' = 1$

5th  $J = 1$ ,  $K = 1 \rightarrow Q = 1, Q' = 0$

6th  $J = 0$ ,  $K = 1 \rightarrow Q = 0, Q' = 1$

### Question 2

$Q_B$	$Q_A$
0	0
0	1
1	0
0	0

So, it has to be a mod 3 counter

**Question 3**Applications of Flip Flops

- Registers
- Memory
- Data storage
- Data transfer

Applications of Counters

- Frequency counters
- Digital clock
- Time measurement