

VLSI System Design

ELE301P

LAB - 7 - Report

Praveen B R

COE19B007

Submission Date: 27/10/2021

INDEX

❖ Q1) Arithmetic Logic Unit (8bit)

- Objective
- Theory
- Code
- Output/Waveform
- Conclusion
- Application

❖ Miscellaneous Questions

- Question 1
- Question 2

Q1)

Objective:

To design and implement an 8bit Arithmetic Logic Unit (ALU) in Verilog with the given operations.

Theory:

An ALU (Arithmetic Logic Unit) is a digital electronic circuit which conducts operations on binary numbers in arithmetic and bitwise logical ways. The latter operates on binary numbers in terms of individual bits whilst numbers are covered through the arithmetic processes.

For the given assignment I decided to design an ALU for 8 bit input numbers to perform given tasks based on select line.

Code:

```
module alu8(a, b, sel, out, cf, zf, nf, pf, of);
    input [7:0] a, b;
    input [3:0] sel;
    output cf, zf, nf, pf, of;
    reg zf, pf, of;
    output [7:0] out;
    integer count;
    reg [8:0] a_reg;
    reg [8:0] result;
    wire temp;

    assign out = result[7:0];
    assign cf = result[8];
    assign nf = result[7];

    always @(*)
    begin
        zf = 1'b0;
        pf = 1'b0;
        of = 1'b0;
        case (sel)
            4'd0:
                result = a + b; // Addition
            4'd1:
                result = a - b; // Subtraction
            4'd2:
                result = a * b; // Multiplication
            4'd3:
```

```

        result = a / b; // Division
4'd4:
        result = a & b; // Bitwise AND
4'd5:
        result = a | b; // Bitwise OR
4'd6:
        result = a ^ b; // Bitwise XOR
4'd7:
        result = ~(a | b); // Bitwise NAND
4'd8:
        result = ~(a & b); // Bitwise NOR
4'd9:
        result = ~(a ^ b); // Bitwise XNOR
4'd10:
        result = a << b; // Left Shift
4'd11:
        result = a >> b; // Right shift
4'd12:
        begin // Rotate Left with Carry
            a_reg = a;
            for(integer i = 0; i < b; i++)
            begin
                a_reg = {a_reg[7:0], a_reg[8]};
            end
            result = a_reg;
        end
4'd13:
        begin // Rotate Right with Carry
            a_reg = {a[7:0], 1'b0};
            for(integer i = 0; i < b; i++)
            begin
                a_reg = {a_reg[0], a_reg[8:1]};
            end
            a_reg = {a_reg[0], a_reg[9:1]};
            result = a_reg;
        end
4'd14:
        result = (a == b) ? 8'd1 : 8'd0;
endcase

```

```

        if(out == 8'd0)
            zf = 1'b1;

        count = 1'b0;
        for(integer j = 0; j < 8; j++) begin
            if(result[j] == 1'b1)
                count++;
        end
        if(count % 2 == 0)
            pf = 1'b1;

        if(a[7] == b[7]) begin
            if(result[7] != a[7])
                of = 1'b1;
        end
    end
endmodule

module alu8_tb;
    reg[7:0] a, b;
    reg[3:0] sel;

    wire[7:0] out;
    wire cf, zf, nf, pf, of;

    alu8 alu1(a, b, sel, out, cf, zf, nf, pf, of);
    initial begin
        a = 8'b10101010;
        b = 8'b11110000;
    end
    initial begin
        #0      sel=4'b0000;
        #14     $finish;
    end
    always begin
        #1 sel += 1;
    end
    initial begin
        $dumpfile("alu8.vcd");
    end
endmodule

```

```

$dumpvars(0,alu8_tb);

$monitor(" a=%b b=%b sel=%d out=%b carry=%b zf=%b nf=%b
pf=%b of=%b", a, b, sel, out, cf, zf, nf, pf, of);

end

endmodule

```

Output/Waveform:


Terminal

```

PS E:\Sem 5\VLSI\Lab\lab7> iverilog 8alu.v
PS E:\Sem 5\VLSI\Lab\lab7> vvp a.out
VCD info: dumpfile alu8.vcd opened for output.
a=11110000 b=10101010 sel= 0 out=10011010 carry=1 zf=0 nf=1 pf=1 of=0
a=11110000 b=10101010 sel= 1 out=01000110 carry=0 zf=0 nf=0 pf=0 of=1
a=11110000 b=10101010 sel= 2 out=01100000 carry=1 zf=0 nf=0 pf=1 of=1
a=11110000 b=10101010 sel= 3 out=00000001 carry=0 zf=0 nf=0 pf=0 of=1
a=11110000 b=10101010 sel= 4 out=10100000 carry=0 zf=0 nf=1 pf=1 of=0
a=11110000 b=10101010 sel= 5 out=11111010 carry=0 zf=0 nf=1 pf=1 of=0
a=11110000 b=10101010 sel= 6 out=01011010 carry=0 zf=0 nf=0 pf=1 of=1
a=11110000 b=10101010 sel= 7 out=00000101 carry=1 zf=0 nf=0 pf=1 of=1
a=11110000 b=10101010 sel= 8 out=01011111 carry=1 zf=0 nf=0 pf=1 of=1
a=11110000 b=10101010 sel= 9 out=10100101 carry=1 zf=0 nf=1 pf=1 of=0
a=11110000 b=10101010 sel=10 out=00000000 carry=0 zf=1 nf=0 pf=1 of=1
a=11110000 b=10101010 sel=11 out=00000000 carry=0 zf=1 nf=0 pf=1 of=1
a=11110000 b=10101010 sel=12 out=11000011 carry=0 zf=0 nf=1 pf=1 of=0
a=11110000 b=10101010 sel=13 out=00111100 carry=0 zf=0 nf=0 pf=1 of=1
8alu.v:108: $finish called at 14 (1s)
a=11110000 b=10101010 sel=14 out=00000000 carry=0 zf=1 nf=0 pf=1 of=1

```

Waveform

 

Conclusion:

Thus, an 8bit Arithmetic Logic Unit (ALU) has been designed and implemented in Verilog with the given operations.

Application:

ALU is stands for **arithmetic and logical unit** which performs all arithmetic operations like **addition, subtraction, division and multiplication** and **logical operations** of the computer system. It works the coordination of **control unit** and **memory unit**. It is the **building block** of CPU. Modern CPU contains strong and most complex ALUs and modern CPUs holds a control unit

Miscellaneous Questions

Question 1 Explain the following data types in verilog

a) WAND

Wand is a net type variable which can take multiple values and perform AND operation on them and give the Output.

b) WOR

Wor is a net type variable which can take multiple values and perform OR operation on them and give the Output.

Code for WAND,WOR

```
module Type_wand(A,y);
input A;
output y;
wand k;
supply0 B;
assign k = A & B;
assign k = A | B;
assign y = k;
endmodule
```

```
module Type_wor(A,y);
input A;
output y;
wor k;
supply1 B;
assign k = A & B;
assign k = A | B;
assign y = k;
endmodule
```

```
module oq_tb;
reg A,B;
wire x,y;
Type_wor t1(A,x);
Type_wand t2(B,y);
initial
begin
A = 1;
```

```

B = 1;
end
initial
begin
$monitor("WOR      A=%b x=%b\nWAND      B=%b y=%b",A,x,B,y);
end
endmodule

```

c) TRI

TRI statement used to for assign different values to a same variable based on the state of assigning values

```

module Type_tri (A,B,y);
input A,B;
output y;
tri z;
assign z = A;
assign z = B;
assign y = z;
endmodule

module test;
reg A,B;
wire y;
Type_tri t1(A,B,y);
initial
begin
#10 A = 1;B= 1'bz;
#10 A = 1'bz ;B =0;
end
initial
begin
$monitor("A = %b B =%b y = %b",A,B,y);
end
endmodule

```

d) Supply0

Supply0 are the wires tied to ground or logical value 0.ada

e) Supply1

Supply1 are the wires tied to power or logical value 1.

```

module supply_type(Output);

```



```

    output Output;
    supply0 A;
    supply1 B;

    assign Output = A | B;
endmodule

module supply_tb();
    wire Output;

    supply_type S1 (Output);

    initial begin
        $monitor ("Output=%b",Output);
    end
endmodule

```

Question 2 What is task statement?

- ☐ Task is a general statement and can calculate multiple result values and return them using **output** and **input** type arguments.
- ☐ Tasks can contain time-consuming simulation elements such as @, posedge, and others. Tasks are used in all programming languages, generally known as procedures or subroutines.
- ☐ Included in the main body of code, they can be called many times, reducing code repetition

```

module q3_tb;
    reg [2:0] A,B,Sum;
    task add;
    input [2:0] A;
    input [2:0] B;
    output [2:0] Sum;
    begin
        Sum = A + B;
    end
endtask
initial
begin

```

```
A = 3'b100;B = 3'b001;  
add(A,B,Sum);  
end  
initial  
begin  
$monitor("A = %b = %b Sum=%b",A,B,Sum);  
end  
endmodule
```