

VLSI System Design

ELE301P

LAB - 9 - Report

Praveen B R

COE19B007

Submission Date: 13/11/2021

INDEX

- ❖ Q1) Lift Design
 - Objective
 - Theory
 - Code
 - Output/Waveform
 - Conclusion


- ❖ Miscellaneous Questions
 - Question 1
 - Question 2
 - Question 3

Q1) Lift Design

Objective:

To design a lift group system consisting of 4 lifts which serves for a 10 story building such that waiting time is minimum.

Theory:

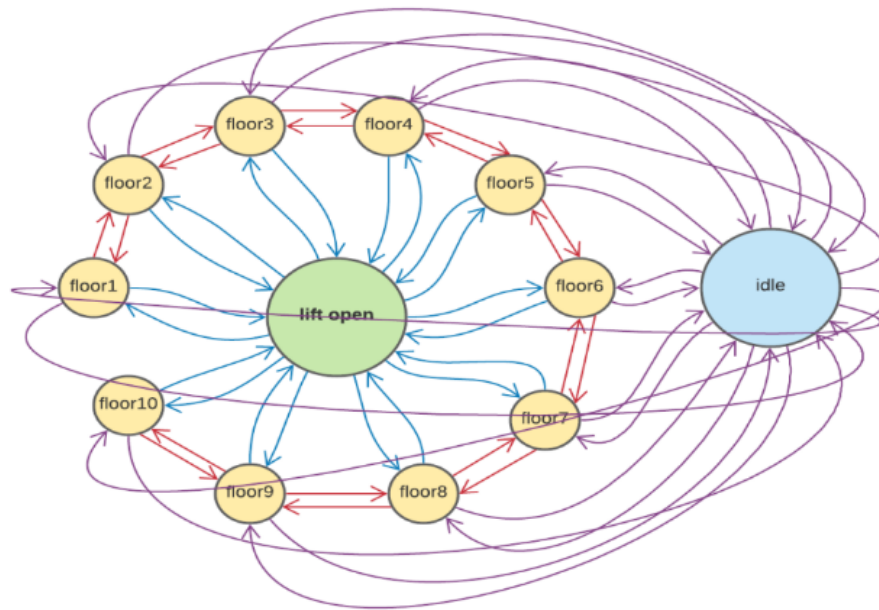

Here, I need to design a lift system consisting of 4 lifts which will be used in a building of 10 floors in such a way that that waiting time is minimum.

My logic is that waiting time is calculated for each floor and to achieve the minimum average waiting time I decided to place lifts on floors 1,4,7,10.

Floor	Waiting Time
1	0
2	1
3	1
4	0
5	1
6	1
7	0
8	1
9	1
10	0

Average Waiting Time = 0.6 units

Lift 1 is on floor 1

Lift 2 is on floor 4
 Lift 3 is on floor 7
 Lift 4 is on floor 10

Implementing it in verilog

Code:

```
module Lift_Controller(floor, lift_number);
    input wire [3:0] floor;
    output reg [2:0] lift_number;
    integer count=0, wt=0;

    always @(floor) begin
        if(floor<3) lift_number = 1;
        else if(floor>2 && floor<6) lift_number=2;
        else if(floor>5 && floor<9) lift_number=3;
        else if(floor>8 && floor<11) lift_number=4;

    end

    always @(floor) begin
        count=count+1;
        if(floor==1 || floor==4 || floor==7 || floor== 10)
            wt = 0;
        else
            wt = 1;
        $strobe("waiting time for floor %d      = %d",count,wt);
    end
endmodule

module lift_tb;
    reg [3:0] floor;
    wire [2:0] lift_number;

    initial begin
        floor=1; #5 // ground floor
        floor=2; #5
        floor=3; #5
        floor=4; #5
        floor=5; #5
    end
endmodule
```

```

        floor=6; #5
        floor=7; #5
        floor=8; #5
        floor=9; #5
        floor=10; #5 // top floor
        $display("\nAvg waiting time = 0.6");
    $finish;
end

Lift_Controller LC1 (floor, lift_number);
initial
begin
    $dumpfile("lift.vcd");
    $dumpvars(0, lift_tb);
end
initial
begin
    $monitor("\nThe floor calling lift = %d ; The name of the lift
arrived = %d", floor, lift_number);
end

endmodule

```

Output/Waveform:

Terminal

```

PS E:\Sem 5\VLSI\Lab\lab 9> iverilog lift.v
PS E:\Sem 5\VLSI\Lab\lab 9> vvp a.out

The floor calling lift = 1 ; The name of the lift arrived = 1
waiting time for floor      1      =      0

The floor calling lift = 2 ; The name of the lift arrived = 1
waiting time for floor      2      =      1

The floor calling lift = 3 ; The name of the lift arrived = 2
waiting time for floor      3      =      1

The floor calling lift = 4 ; The name of the lift arrived = 2
waiting time for floor      4      =      0

The floor calling lift = 5 ; The name of the lift arrived = 2
waiting time for floor      5      =      1

The floor calling lift = 6 ; The name of the lift arrived = 3
waiting time for floor      6      =      1

The floor calling lift = 7 ; The name of the lift arrived = 3
waiting time for floor      7      =      0

The floor calling lift = 8 ; The name of the lift arrived = 3
waiting time for floor      8      =      1


The floor calling lift = 9 ; The name of the lift arrived = 4
waiting time for floor      9      =      1

The floor calling lift = 10 ; The name of the lift arrived = 4
waiting time for floor     10      =      0

Avg waiting time = 0.6
lift.v:41: $finish called at 50 (1s)
PS E:\Sem 5\VLSI\Lab\lab 9>


```

Waveform

 

Conclusion:

Thus, a lift group system consisting of 4 lifts which serves for a 10 story building such that waiting time is minimum has been successfully implemented.

 Miscellaneous Questions**Question 1 What is the output sequence for the given input data sequence 001010110110110111?**

Let us name the state 0/0 as A and 1/1 as B.

Since the start state is not mentioned in the above figure, we will find the output sequence for both A and B as the start states.

If we consider A as the start state, then for the input sequence 001010110110110111 we get output as 001100100100100101.

If we consider B as the start state, then for the input sequence 001010110110110111 we get output as 110011011011011010.

Question 2 What is the behaviour of the above Finite state machine?

Clearly, outputs of the FSM are given **inside** the states so we can say that it only depends on the current state. So the given FSM is of Moore type.

Question 3 Decide the Flip-flop which can be used by avoiding external logic gates.

We can represent the given FSM by avoiding external logic by using D flip flop as it gives high out when input is high and low out when input is low

D Flip Flop		
Input	Output	
D	Q	Q^{\wedge}
0	0	1
1	1	0