

VLSI System Design

ELE301P

LAB - 2 - Report

Praveen B R

COE19B007

Submission Date: 01/09/2021

# INDEX

## 4x4 Array Multiplier

- Structural Modelling
  - Code
  - Waveform
- Behavioural Modelling
  - Code
  - Waveform

## Other Questions

- Question 1
- Question 2
- Question 3

## Implement 4\*4 array multiplier

### **Objective:**

To implement 4\*4 array multiplier in Verilog using,


- Structural modelling
- Behavioural modelling

### **Theory:**

Array multiplier is used to perform the arithmetic operations. The design structure of the array Multiplier is regular, it is based on the add shift algorithm principle.

$$\text{Partial product} = \text{the multiplicand} * \text{multiplier bit}$$

 where AND gates are used for the product, the summation is done using Full Adders and Half Adders where the partial product is shifted according to their bit orders. The 4×4 array multiplier shown below has two 4 inputs and 8 output,



### **Structural Modelling:**

#### **Code**

```
module fa(a,b,cin,sum,cout); //module for full adder
    input a,b,cin;
    output cout,sum;

    wire s1,s2,s3;
    xor(s1,a,b);
    and(s2,a,b);
    xor(sum,s1,cin);
    and(s3,s1,cin);
    or(cout,s3,s2);
endmodule
```

```

module rca(A,B,Cin,Cout,Sum); //module for product carry adder
    input [3:0]A,B;
    input Cin;
    output [3:0]Sum;
    output Cout;
    wire t[3:0];
    fa f1(A[0],B[0],Cin,Sum[0],t[0]);
    fa f2(A[1],B[1],t[0],Sum[1],t[1]);
    fa f3(A[2],B[2],t[1],Sum[2],t[2]);
    fa f4(A[3],B[3],t[2],Sum[3],Cout);
endmodule

```

```

module mul(A,B,Product); //module for 4*1 multiplier
    input [3:0]A;
    input B;
    output [3:0]Product;

    and a1(Product[3],A[3],B);
    and a2(Product[2],A[2],B);
    and a3(Product[1],A[1],B);
    and a4(Product[0],A[0],B);
endmodule

```

```

module am_structural(A,B,Sum); //main module
    input [3:0]A,B;
    output [7:0]Sum;
    wire [3:0]t1,t2,s1,t3,t4,t5,s2,t6,s3;
    wire [3:0]Cout;
    wire cin=1'b0;

    and a1(Sum[0],A[0],B[0]);
    and a2(t1[0],A[1],B[0]);
    and a3(t1[1],A[2],B[0]);
    and a4(t1[2],A[3],B[0]);
    assign t1[3]=0;

    mul m1(A,B[1],t2); //first rca program
    rca f1(t1,t2,cin,Cout[0],s1);
    assign Sum[1] = s1[0];
    assign t5 = {Cout[0],s1[3:1]};

```

```

mul m2(A,B[2],t3); //second rca program
rca f2(t5,t3,cin,Cout[1],s2);
assign Sum[2] = s2[0];
assign t6 = {Cout[1],s2[3:1]};

mul m3(A,B[3],t4); //third rca program
rca f3(t6,t4,cin,Cout[2],s3);
assign Sum[6:3] = s3;
assign Sum[7] = Cout[2];
endmodule

module am_structural_tb; //test_bench
reg [3:0]A,B;
wire [7:0]Product;

am_structural product(A,B,Product);
initial
begin
    #0 A=4'b0000;B=4'b0001;
    #75 $finish;
end
initial
begin
    $dumpfile ("q1.vcd");
    $dumpvars (0,am_structural_tb);
end
initial
begin
    $monitor("num1=%d num2=%d Product=%d",A,B,Product);
end
always
begin
    #5 A = A + 1;
end
always
begin
    #15 B = B + 3;
end
endmodule

```


## Output Terminal

```

PS E:\Sem 5\VLSI\Lab\lab2> iverilog -o q1 q1.v
PS E:\Sem 5\VLSI\Lab\lab2> vvp q1
VCD info: dumpfile q1.vcd opened for output.
num1= 0 num2= 1 Product= 0
num1= 1 num2= 1 Product= 1
num1= 2 num2= 1 Product= 2
num1= 3 num2= 4 Product= 12
num1= 4 num2= 4 Product= 16
num1= 5 num2= 4 Product= 20
num1= 6 num2= 7 Product= 42
num1= 7 num2= 7 Product= 49
num1= 8 num2= 7 Product= 56
num1= 9 num2=10 Product= 90
num1=10 num2=10 Product=100
num1=11 num2=10 Product=110
num1=12 num2=13 Product=156
num1=13 num2=13 Product=169
num1=14 num2=13 Product=182
q1.v:94: $finish called at 75 (1s)
num1=15 num2= 0 Product= 0
PS E:\Sem 5\VLSI\Lab\lab2> gtkwave q1.vcd

```

## Waveform

 

## Behavioural Modelling:

### Code

```

module am_behavioural (A,B,Sum); //main module
    input [3:0] A,B;
    output reg[7:0] Sum;

    reg[5:0][3:0] t;
    reg[3:0][4:0] s;
    reg[2:0] cout;

    always@ (A,B)
    begin
        t[0] = Product(A,B[0]);
        t[1] = Product(A,B[1]);
        Sum[0] = t[0][0];
        s[0] = t[1] + {1'b0,t[0][3:1]};
        t[2] = Product(A,B[2]);
        t[3] = Product(A,B[3]);
        s[1] = t[2] + s[0][4:1];
        s[2] = t[3] + s[1][4:1];
        Sum[1] = s[0][0];
        Sum[2] = s[1][0];
        Sum[7:3] = s[2];
    end

    function [3:0] Product(input [3:0] C,D);
        begin
            Product[3] = C[3]&D;
            Product[2] = C[2]&D;
            Product[1] = C[1]&D;
            Product[0] = C[0]&D;
        end
    endfunction

```

```
endmodule

module am_behavioural_tb;    //test_bench
    reg [3:0]A,B;
    wire [7:0]Product;

    am_behavioural_product(A,B,Product);
    initial
    begin
        #0 A=4'b0000;B=4'b0000;
        #30 $finish;
    end
    initial
    begin
        $dumpfile ("q2.vcd");
        $dumpvars (0,am_behavioural_tb);
    end
    initial
    begin
        $monitor("num1=%d num2=%d Product=%d",A,B,Product);
    end
    always
    begin
        #2 A = A + 1;
    end
    always
    begin
        #6 B = B + 3;
    end
endmodule
```



## Output Terminal


```
PS E:\Sem 5\VLSI\Lab\lab2> iverilog -o q2 q2.v
PS E:\Sem 5\VLSI\Lab\lab2> vvp q2
VCD info: dumpfile q2.vcd opened for output.
num1= 0 num2= 0 Product= 0
num1= 1 num2= 0 Product= 0
num1= 2 num2= 0 Product= 0
num1= 3 num2= 3 Product= 9
num1= 4 num2= 3 Product= 12
num1= 5 num2= 3 Product= 15
num1= 6 num2= 6 Product= 36
num1= 7 num2= 6 Product= 42
num1= 8 num2= 6 Product= 48
num1= 9 num2= 9 Product= 81
num1=10 num2= 9 Product= 90
num1=11 num2= 9 Product= 99
num1=12 num2=12 Product=144
num1=13 num2=12 Product=156
num1=14 num2=12 Product=168
q2.v:47: $finish called at 30 (1s)
num1=15 num2=15 Product=225
PS E:\Sem 5\VLSI\Lab\lab2> gtkwave q2.vcd
```

GTKWave Analyzer v3.3.108 (w)1999-2020 BSI

[0] start time.

[30] end time.

## Waveform

 

## Conclusion:

Thus, 4\*4 array multipliers have been implemented successfully using Verilog in Structural style and Behavioural style.

## Other Questions

**Q1) There is a conditional operator in verilog which can be used as follows: if the given condition is true then a given value will be assigned to the variable and if false other user defined value will be assigned. There is a similar operator in C. Find the verilog operator and its syntax**

Ans:

The described operator is called **Conditional Operator** in verilog also.

Syntax : ***Condition?Expression1:Expression2;***

eg : assign a = (0)?8:9; // 9 will be assigned to a

If the condition is true, expression 1 will be executed else expression 2 will be executed.


**Q2) Find the functionality and use of verilog keyword “parameter”**

Ans:

Parameter keyword in verilog is used to define constants, they do not belong to any other data type such as register or net data types. Value of a parameter can be changed using defparam.

**Q3) In this experiment you have implemented 4\*4 array multiplier. Now draw the logic diagram representation for 4\*3 array multiplier.**

Ans:

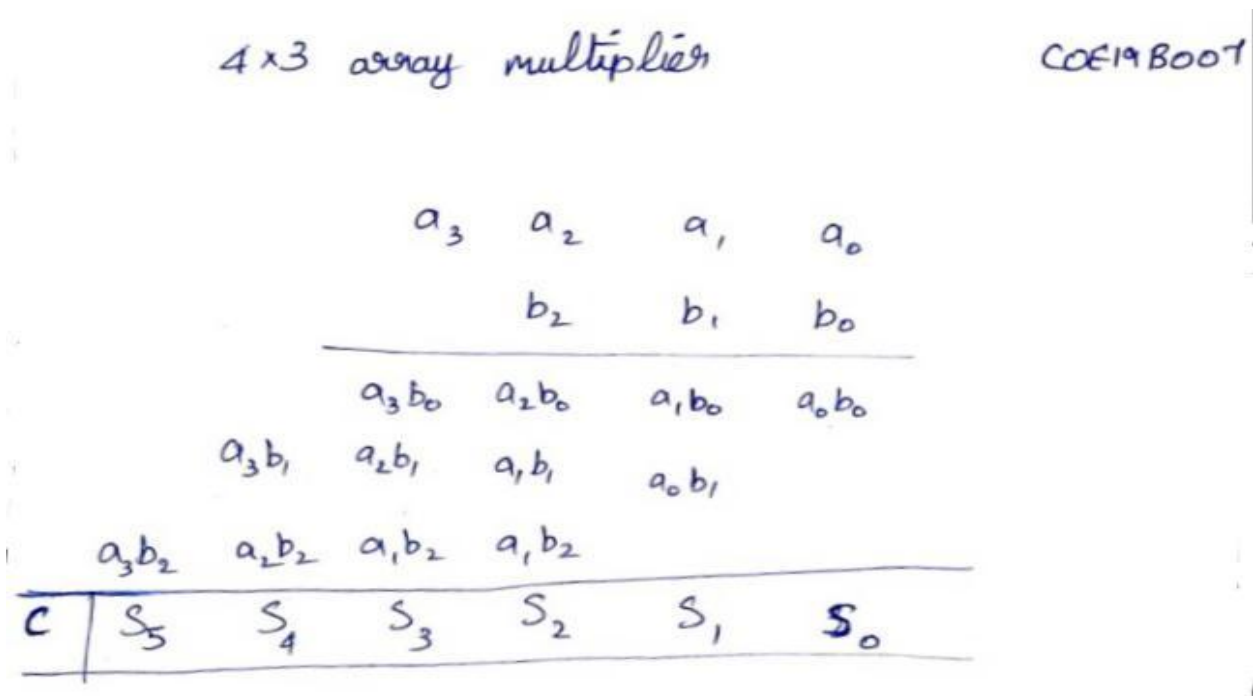

Logic  
Diagram

